#### Lecture 5

# Simple Linear and Nonlinear System

#### Hai-Qing Lin

Beijing Computational Science Research Center


This PowerPoint Notes Is Based on the Textbook 'An Introduction to Computer Simulation Methods: Applications to Physical Systems', 2nd Edition, Harvey Gould and Jan Tobochnik, Addison-Wesley(1996); "A First Course in Computational Physics"; "Numerical Recipes"; "Elementary Numerical Analysis"; "Computational Methods in Physics and Engineering".

# Required for Lecture 5

- \* SHM, periodic motion, oscillatory motion, frequency, amplitude, phase.
- Conservative / dissipative systems.
- Similarities between physical systems.
- Program: SHO, rc; and Solution of forced oscillator with damping
- Comparison of algorithms.
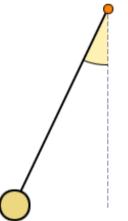
# **Question and Objectives**

- Pendulum, g.
- Day, week, month, year, etc.
- Electric circuit and mechanical system, are they the same?



# Simple Harmonic Motion (SHM, SHO)


#### **Periodic Motion:**

motion that repeats itself at definite time intervals, e.g., earth arounds the sun.

# Oscillatory Motion:

an object undergoes periodic motion between two limits over the same path.

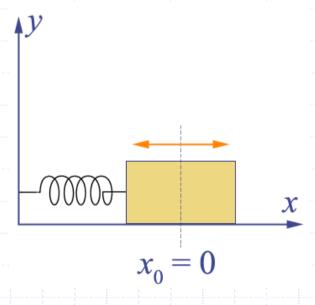**Example:** mass *m* connected to a massless spring.




# Hooke's Law and Equation of Motion

$$F = -k (x - x_0) \leftarrow Approximation?$$

 $x_0$ : equilibrium position,

k: force constant.
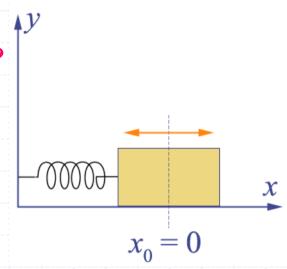
$$\frac{d^{2}x}{dt^{2}} = \frac{F}{m} = -\frac{k}{m}(x - x_{0}) = -\omega_{0}^{2}x$$



 $\omega_0^2 = k/m$  (intrinsic property of the system)

This is a *linear* differential equation describing *simple* harmonic motion. Its solution can be written as

$$x(t) = A \cos(\omega_0 t + \delta)$$
 (direct check?)

A: amplitude,  $\delta$ : phase

### **Harmonic Motion**

• Period T: smallest time for repeated motion

$$x(t+T)=x(t), \quad T=\frac{2\pi}{\omega_0}=\frac{2\pi}{\sqrt{k/m}}$$

- Frequency  $\nu$ : number of cycles per second,  $\nu = 1/T$ .
- **Conservation of total energy** *E*:

$$E = \frac{1}{2}mv^2 + \frac{1}{2}kx^2 = \frac{1}{2}kA^2 = \text{constant}$$

### **Numerical Simulation of SHO**

The following program computes the time dependence of the position and the velocity of a linear harmonic oscillator using *Euler-Richardson* algorithm. One can put a check for **energy conservation** in easily.

# PROGRAM SHO IMPLICIT NONE real :: x,v,w2,t,dt,dt2,tmax integer :: counter,nshow CALL initial(x,v,t,w2,dt,dt2,tmax,nshow) counter=0

DO WHILE (t <= tmax)

CALL update(x,v,w2,t,dt,dt2)

counter = counter + 1

if ( mod(counter,nshow) == 0 ) then

CALL output(x,v,t)

end if

END DO

**END PROGRAM SHO** 

#### **SUBROUTINE initial**(x\_0,v\_0,t,w2,dt,dt2,tmax,nshow)

#### **IMPLICIT NONE**

real :: x = 0, v = 0, t, w2, dt, dt2, tmax, show time

integer :: nshow

write(6,\*) 'Enter Initial: x\_0,v\_0,t,tmax' read(5,\*) x\_0,v\_0,t,tmax

write(6,\*) 'Enter k/m, time step, show\_time' read(5,\*) w2,dt,show\_time

dt2=0.5\*dt nshow=int(show\_time/dt) write(6,1002) 1002 format(2x,'Time',5x,'Position',6x,'Velocity'/)

#### **END SUBROUTINE** initial

#### **SUBROUTINE update**(x,v,w2,t,dt,dt2) ! Euler-Richardson

#### **IMPLICIT NONE**

real :: x,v,w2,t,dt,dt2

real :: acceleration, vmid, xmid

acceleration = -w2\*x

vmid = v + acceleration\*dt2

xmid = x + v\*dt2

acceleration = -w2\*xmid

v = v + acceleration\*dt

x = x + vmid\*dt

t = t + dt

#### **END SUBROUTINE update**

#### **SUBROUTINE** output(x,v,t)

**IMPLICIT NONE** 

real :: x,v,t

write(6,1004) t,x,v

1004 format(f6.3,2f13.6)

#### **END SUBROUTINE output**

# The Simple Pendulum


#### Equation of Motion:

$$v = L\frac{d\theta}{dt} = L\omega,$$

$$a = L\frac{d^2\theta}{dt^2} = L\alpha$$

$$v = L\frac{d\theta}{dt} = L\omega, \qquad a = L\frac{d^{2}\theta}{dt^{2}} = L\alpha$$
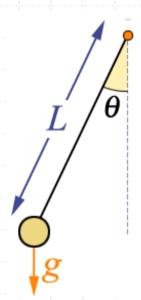
$$mL\frac{d^{2}\theta}{dt^{2}} = -mg\sin\theta, \quad \frac{d^{2}\theta}{dt^{2}} = -\frac{g}{L}\sin\theta$$



This is a *nonlinear* equation due to

$$\sin \theta = \theta - \frac{\theta^3}{3!} + \dots + (-1)^n \frac{\theta^{2n+1}}{(2n+1)!} + \dots$$

# The Simple Pendulum

For sufficiently small  $\theta$ ,  $\sin \theta \approx \theta$ , we have

$$\frac{d^2\theta}{dt^2} = -\frac{g}{L}\theta,$$

 $\frac{d^2\theta}{dt^2} = -\frac{g}{I}\theta, \qquad \theta << 1, \text{measured in radians}$ 

Thus this is a SHO with  $T = 2\pi \sqrt{L/g}$ 

$$T = 2\pi \sqrt{L/g}$$

If  $\theta$  is not small, then how to solve this equation?

The system is conserved and the total energy *E* is

$$E = \frac{1}{2}mL^2\left(\frac{d\theta}{dt}\right)^2 + mgL(1 - \cos\theta)$$

# The Simple Pendulum

Then

$$\frac{d\theta}{dt} = \sqrt{\frac{2E - 2mgL(1 - \cos\theta)}{mL^2}}$$

$$\int \frac{d\theta}{\sqrt{2E - 2mgL(1 - \cos\theta)}} = \int \frac{dt}{\sqrt{mL^2}} = \frac{t - t_0}{\sqrt{mL^2}}$$

One can do (numerical) integration to solve this problem.

# **Dissipative System**

SHO belongs to *conservative* systems. In nature, we observe *dissipative* systems and their motions are damped, e.g., drag force and frictional force.

$$\frac{d^2x}{dt^2} = -\omega_0^2 x - \gamma \frac{dx}{dt}$$

where  $\gamma$  is the *damping coefficient* measuring the magnitude of dissipative force.

To keep system moving, one needs external force.

# Response to External Force

When the system subjects to an external force (perturbation), the response of the system reveals the nature of the system. Consider a *driven* damped linear oscillator, the equation of motion is

$$\frac{d^2x}{dt^2} = -\omega_0^2 x - \gamma \frac{dx}{dt} + \frac{1}{m}F(t)$$


We usually calculate the response of the system in terms of the x rather than the v. Force F(t) could have arbitrary forms and usually we do our analysis by **assuming** 

$$F(t) = A_0 \cos{(\omega t)},$$


where  $\omega$  is the angular frequency of the driving force.

# **Commonly Used External Forces**

Half wave driving force

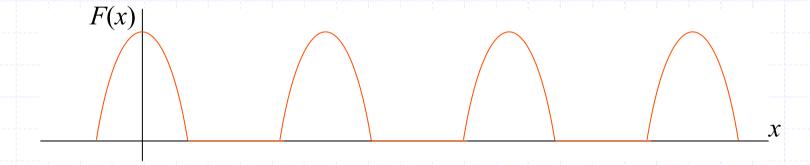

Unit step function

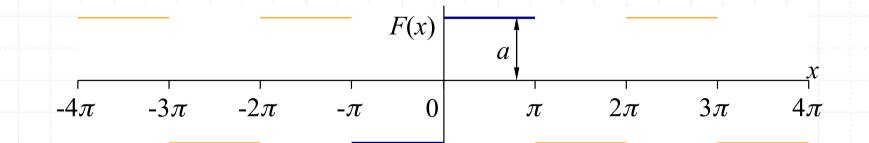

#### **Electrical Circuit Oscillations**

Physics deals with laws of nature. Many seeming different phenomena can be described by the same set of physical laws (equations), e.g. RLC circuit & SHO.

#### **Electrical Circuit:**

Based on *Kirchoff*'s loop rules, came from charge conservation and energy conservation.

| Element   | Voltage Drop    | Units                           |
|-----------|-----------------|---------------------------------|
| Resistor  | $V_R = IR$      | Resistance $R$ , ohms $\Omega$  |
| Capacitor | $V_C = Q/C$     | Capacitance C, farads F         |
| Inductor  | $V_L = L dI/dt$ | Inductance <i>L</i> , henries H |

#### **RLC Circuit**


$$V_L + V_R + V_C = V_s(t)$$

$$L\frac{dI}{dt} + RI + \frac{Q}{C} = V_s(t)$$

$$L\frac{d^{2}Q}{dt^{2}} + R\frac{dQ}{dt} + \frac{Q}{C} = V_{s}(t), \quad I = \frac{dQ}{dt}$$

This equation is identical to the previous equation for driven damped linear oscillator.
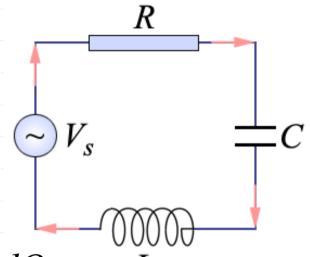
$$\frac{d^2x}{dt^2} + \omega_0^2 x + \gamma \frac{dx}{dt} = \frac{1}{m}F(t)$$




#### Comparisons of Electric Circuit & Mechanical System

# Electric CircuitMechanical SystemCharge QDisplacement xCurrent I = dQ/dtVelocity v = dx/dtInductance LMass mInverse capacitance 1/CSpring constant kResistance RDamping $\gamma$

$$L\frac{d^2Q}{dt^2} + R\frac{dQ}{dt} + \frac{Q}{C} = V_s(t) \quad \frac{d^2x}{dt^2} + \omega_0^2 x + \gamma \frac{dx}{dt} = \frac{1}{m}F(t)$$
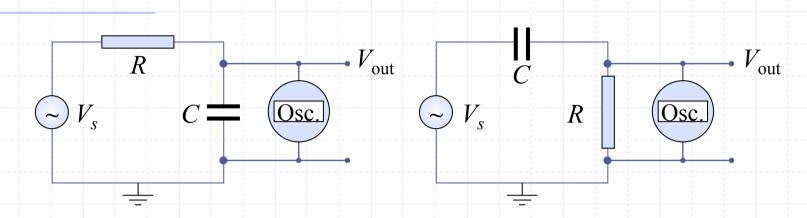
#### Real Measurement vs Computer Simulation



Note that although the loop equations is identical regardless of the order of placement of the electrical elements, the output voltage measured by the oscilloscope could be **different**.

An advantage of a computer simulation of an electrical circuit is that the measurement of a voltage drop across a circuit element does **not affect** the properties of the circuit. In fact, digital computers are often used to optimize the design of circuits for special applications.

# Simulating RC Circuit

Program **rc** simulates an **RC** circuit with an alternating current (ac) voltage source of the form  $V_s(t) = \cos \omega t$ .

**PROGRAM rc**! simulation of RC circuit with ac voltage source LIBRARY "csgraphics"

**CALL initial**(Q,R,tau,V0,omega,tmax,t,dt)

**CALL set\_up\_windows**(#1,#2,V0,tmax)

DO while t <= tmax

**CALL scope**(Q,I,R,tau,V0,omega,dt)

LET t = t + dt

**CALL source\_voltage**(#1,V0,omega,t)

**CALL output\_voltage**(#2,I,R,t)

LOOP

CLOSE #1

CLOSE #2

**END** 

Program details not shown

# **Damped Oscillator**

$$m\frac{d^2x}{dt^2} + \beta\frac{dx}{dt} + kx = 0$$

$$x'' + 2\gamma x' + \omega_0^2 x = 0$$
 with  $\beta/m = 2\gamma$ ,  $k/m = \omega_0^2$ 

x(t)

#### **Over-Damped**

$$\gamma^2 > \omega_0^2$$
, i.e.  $\beta^2 > 4km$   
 $x = e^{-\gamma t} (Ae^{\alpha t} + Be^{-\alpha t})$   
where  $\alpha^2 = \gamma^2 - \omega_0^2$ 



i

# **Damped Oscillator**

$$m\frac{d^2x}{dt^2} + \beta\frac{dx}{dt} + kx = 0$$

$$x'' + 2\gamma x' + \omega_0^2 x = 0$$
 with  $\beta/m = 2\gamma$ ,  $k/m = \omega_0^2$ 

#### **Critically Damped**

$$\gamma^2 = \omega_0^2, \text{ i.e. } \beta^2 = 4km$$
$$x = e^{-\gamma t} (A + Bt)$$



x(t)

 $\gamma^2 = \omega_0^2$ 


# **Damped Oscillator**

$$m\frac{d^2x}{dt^2} + \beta\frac{dx}{dt} + kx = 0$$

$$x'' + 2\gamma x' + \omega_0^2 x = 0 \quad \text{with } \beta/m = 2\gamma, k/m = \omega_0^2$$
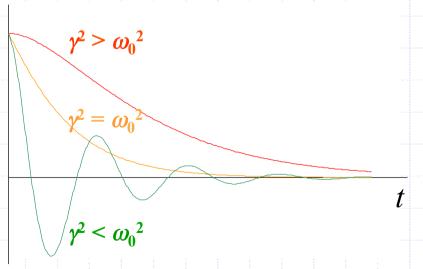
#### **Under-Damped**

$$\gamma^2 < \omega_0^2$$
, i.e.  $\beta^2 < 4km$   
 $x = e^{-\gamma t} (A\sin \lambda t + B\cos \lambda t)$   
 $= Ce^{-\gamma t} \cos(\lambda t - \phi)$   
where  $\lambda^2 = \omega_0^2 - \gamma^2$ 



# Forced Vibrations, $F(t) = F_0 \cos \alpha t$

$$x'' + 2\gamma x' + \omega_0^2 x = f_0 \cos \alpha t$$
  
with  $\beta/m = 2\gamma$ ,  $k/m = \omega_0^2$ ,  $F_0/m = f_0$ 

General solution of  $x'' + 2\gamma x' + \omega_0^2 x = f_0 \cos \alpha t$ 

= general solution of  $x'' + 2\gamma x' + \omega_0^2 x = 0$ 

(transient/homogeneous solution)

+ a particular solution of  $x'' + 2\gamma x' + \omega_0^2 x = f_0 \cos \alpha t$ (steady-state/inhomogeneous solution)

$$x = \frac{f_0}{\sqrt{(\alpha^2 - \omega_0^2)^2 + 4\gamma^2 \alpha^2}} \cos(\alpha t - \phi)$$

where 
$$\tan \phi = \frac{2\gamma\alpha}{\alpha^2 - \omega_0^2}$$
,  $0 \le \phi \le \pi$ 

# **Amplitude Resonance**

• Amplitude A is maximum at resonance frequency  $\alpha_r$  by setting

$$\frac{dA}{d\alpha}\Big|_{\alpha=\alpha_r} = 0$$
, where  $A = \frac{f_0}{\sqrt{(\alpha^2 - \omega_0^2)^2 + 4\gamma^2 \alpha^2}}$ 

$$A_{\text{max}} = \frac{f_0}{2\gamma \sqrt{{\omega_0}^2 - \gamma^2}}$$

$$\alpha_r = \sqrt{{\omega_0}^2 - 2\gamma^2}$$


$$\alpha_r = \sqrt{\omega_0^2 - 2\gamma^2}$$

• For small damping,  $\gamma \to 0$   $A_0 \approx f_0/2\gamma\omega_0 \to \infty$ 
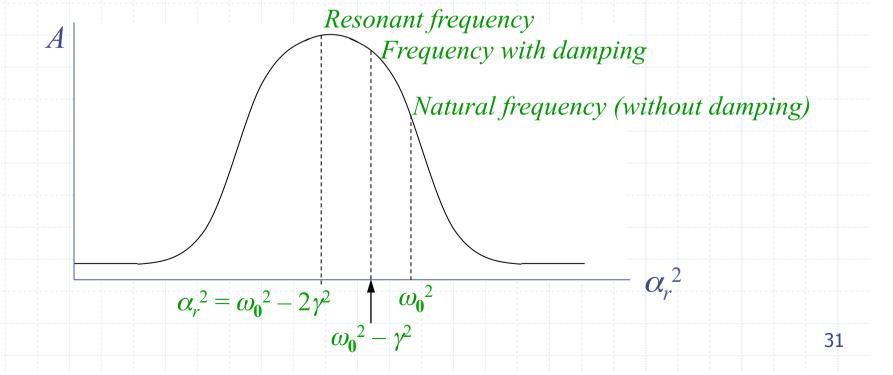
# Plot of A vs $\alpha^2$

• Write the amplitude in terms of  $\alpha_r$ 

$$A = \frac{f_0}{\sqrt{(\alpha^2 - \alpha_r^2)^2 + 4\gamma^2(\omega_0^2 - \gamma^2)}}$$



# Lecture 5 Review and Required

- \* SHM, periodic motion, oscillatory motion, frequency, amplitude, phase.
- Conservative / dissipative systems.
- Similarities between physical systems.
- Program: SHO, rc.
- Comparison of algorithms.
- Damped oscillator.

# **Chemical Oscillations**

$$A + 2B \rightarrow 3B + C$$

Rate equations are:


$$\frac{dA}{dt} = -kAB^2$$

$$\frac{dB}{dt} = kAB^2$$


$$\frac{dt}{dC} = kAB^2$$

# **Commonly Used External Forces**

Half wave driving force (voltage source)

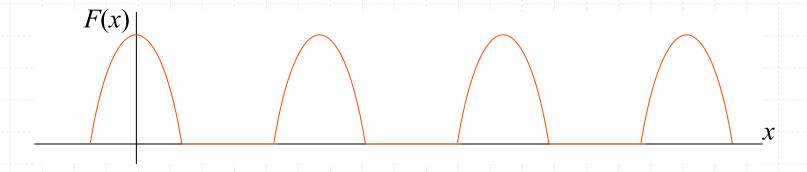


Unit step function

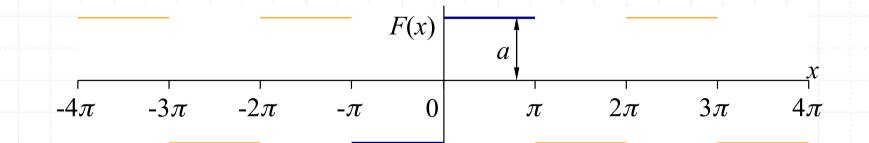
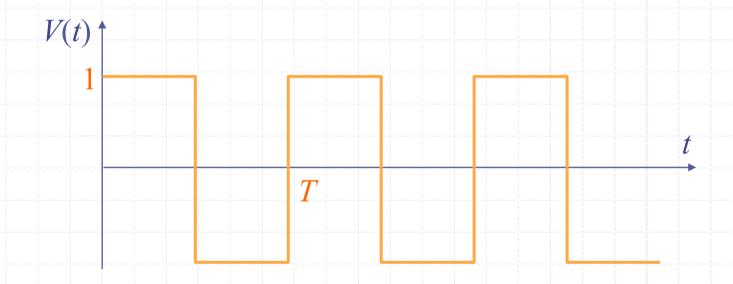
# **Square Wave Input**

Voltage source is a periodic square wave with period *T* and unit amplitude, how to simulate?



We will discuss these in Fourier Transform